



Control System Training

MODULE 5 – Sequential Logic

Copyright Notice

These training materials, including the samples, exercises, and solutions, are copyrighted materials. Any reproduction, or use of any kind without the specific written approval of the author is strictly prohibited.


Permission for extra-curricular use by First FRC teams for FRC related training is granted, provided the original copyright and acknowledgements are retained.

© Jim Simpson, 2018

Sequential Logic


- **Output depends on both state of current inputs and previous input and output states.**

Edge Triggered – ON

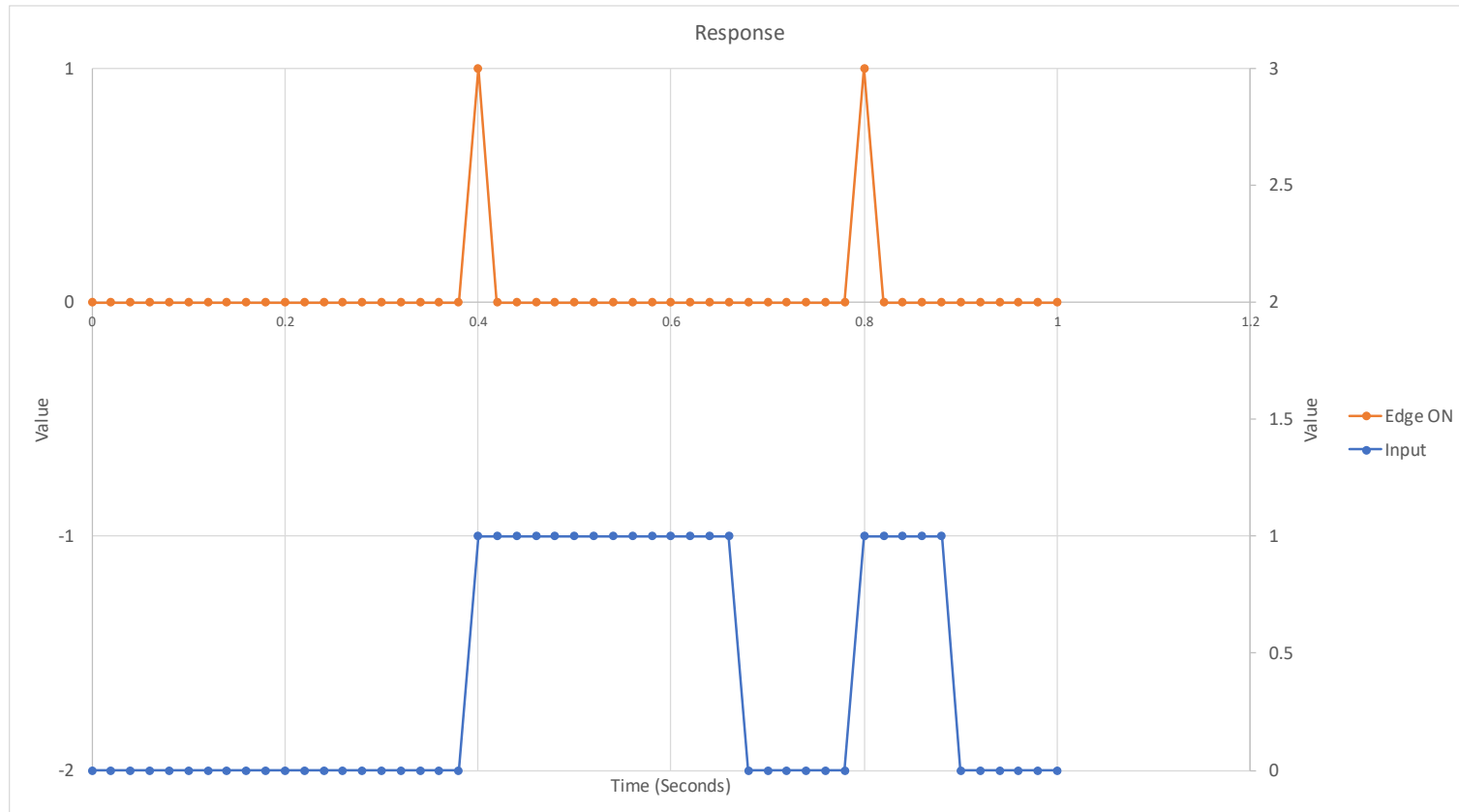


- Only true for a single scan.

Edge Triggered - OFF

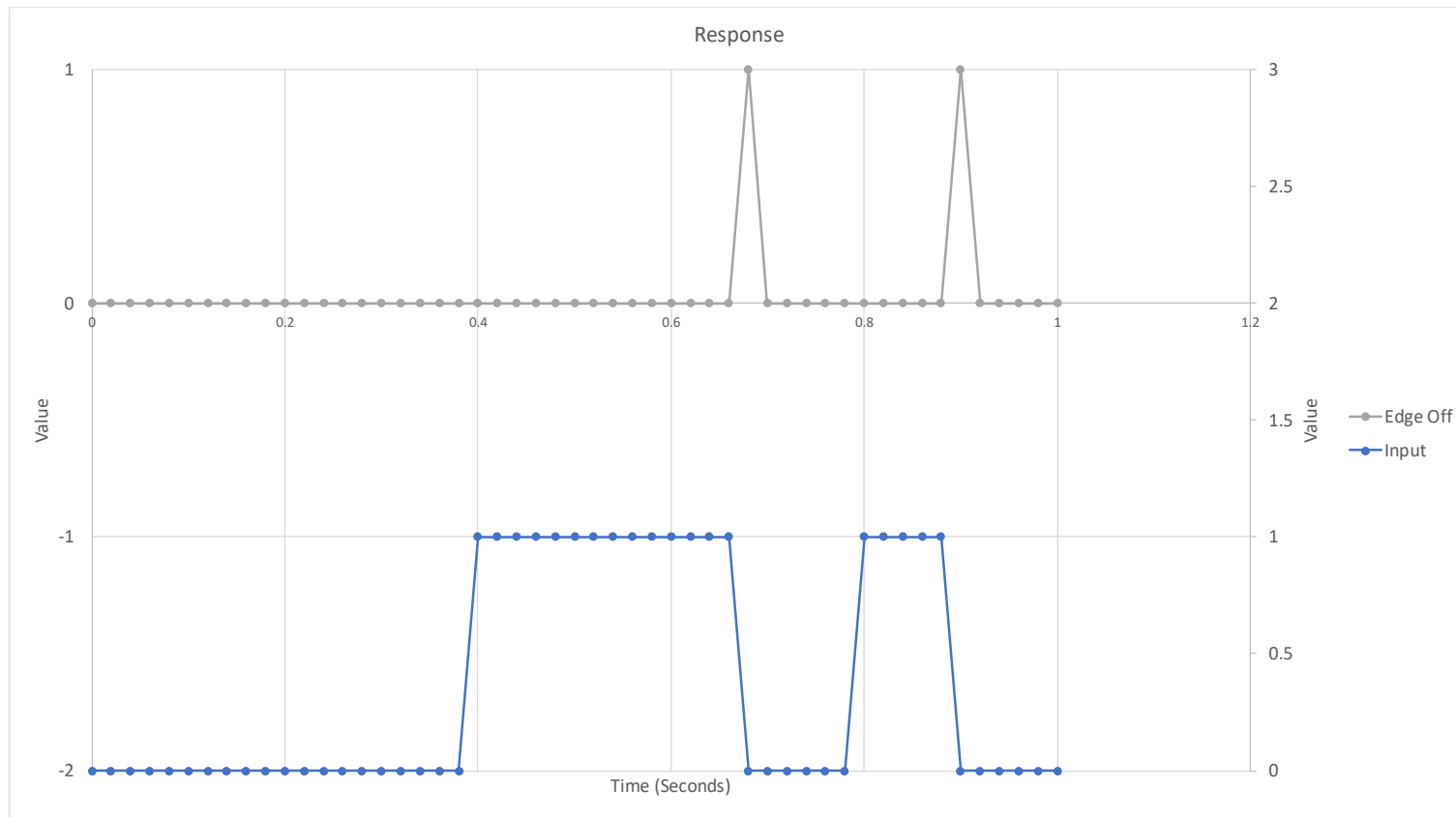


- Only true for a single scan

Edge Triggered - CHANGE

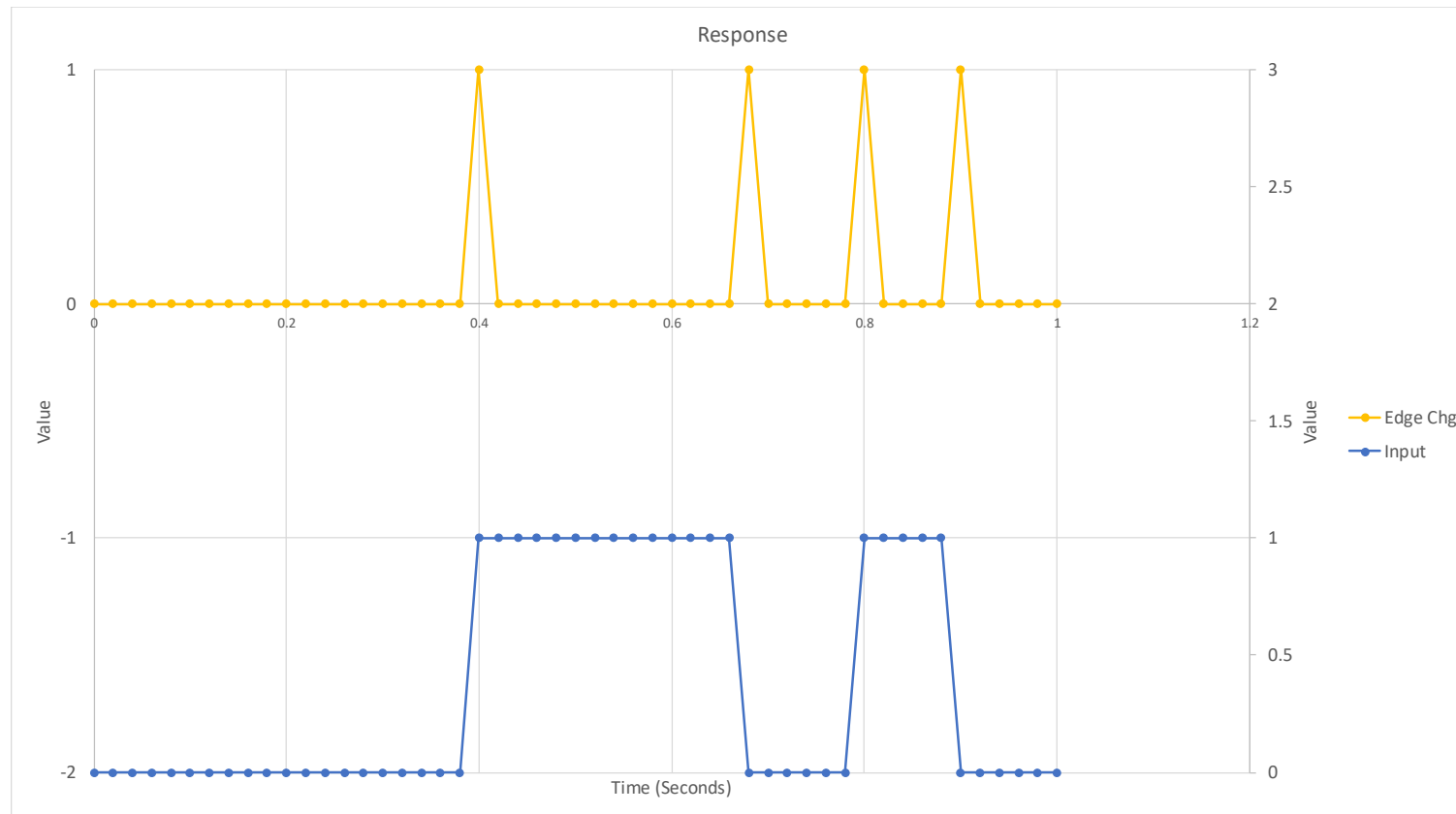

- Only true for a single scan

One Shot

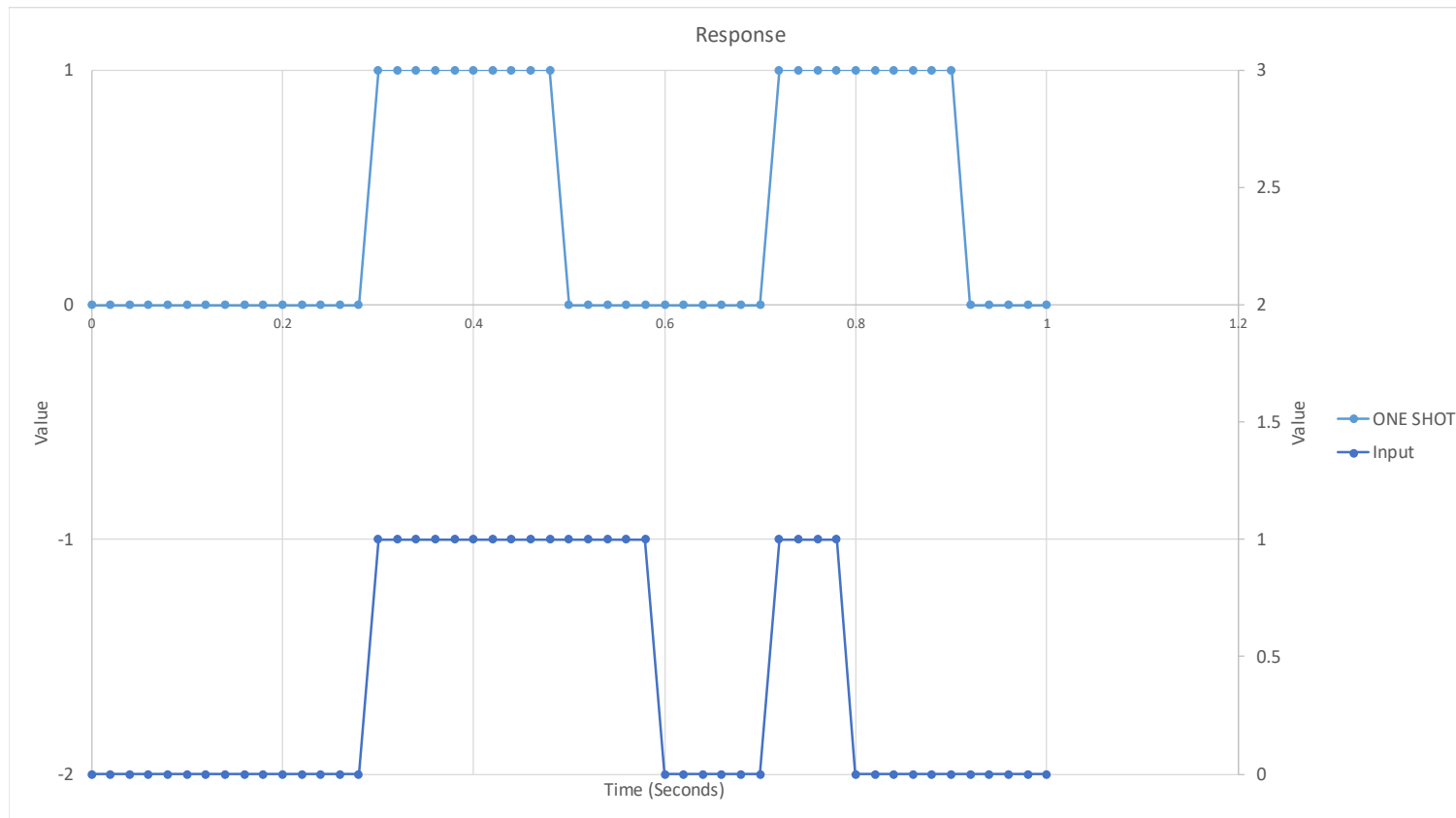


- Oneshot time is 0.200 seconds

On Delay



- **Delay is 0.200 Seconds**
- **If input goes false before delay expires, output is never true.**


Off Delay

 

- Off delay time is 0.080 seconds.

Set / Reset Flip Flop

Set / Reset Flip Flop			
Input			
Set	Reset	Override	Output
1	0	N/A	1
0	1	N/A	0
0	0	N/A	Prev Output
1	1	Set	1
1	1	Reset	0

 

- Can think of this as “Boolean memory”. This is the building block of all computers.
- If both are true at the same time, one overrides the other. This is usually selectable.

Designing Sequential Logic 1/4


□ **Sample Problem – Cube Grab**

- Control system uses a 20 msec loop time
- System is ready when “hand” is opened and “arm” is retracted
- Users pushes button to initiate “cube grab”. Auto repeat of cube grab is not allowed.
- Ensure user pushed button for 60 msec
- Close “arm” extension solenoid. Wait 1 second for arm to extend.
- Close “hand” solenoid. Wait 2.0 seconds for “hand” to settle.
- Open “arm” extension solenoid. Wait 1.3 seconds for arm to retract.
- Open “hand” solenoid to release potential cube into bin. Wait 1.5 seconds for cube to drop before allowing next “grab” action.

□ **Enhancement – Add a cancel button**

Designing Sequential Logic 2/4


□ Draw the Logic Diagram Graph

 

Designing Sequential Logic 3/4

- **Start with inputs**
- **Determine relationships**
 - What inputs does an output relate to
- **Draw Logic Diagram**
- **Add intermediate Logic to Graph**
- **Repeat last two steps if needed to refine logic**

Final Logic Diagram

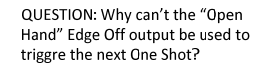

NOTE: The inputs to the FLIP/FLOPs can also be used to perform the solenoid output commands.

Exercise 5.1 - List Programming Objects

- **Create a list of potential objects from this chapter to program.**
 - List the inputs and outputs for each object.

Exercise 5.2 – Shoot frisbee

- **User pushes a button to shoot frisbee.**
- **Ensure user meant to push button. Button must be pressed for three cycles before initiating action. (Cycle time is 0.020 seconds).**
- **Can only shoot a frisbee if we have one. A limit switch indicates this. Also battery voltage must be > 11.5 volts. Can only shoot one frisbee at a time.**
- **Motors take 3 seconds to spin up to speed.**
- **Engage solenoid for 2 second to push frisbee into shooting wheel.**
- **Allow 2 more seconds for shooting to occur.**
- **After shooting is done, stop motor. (For now, don't allow continuous shooting.)**
- **Allow user to press a Cancel button. The cancel button must be pressed for at least 3 cycles before becoming active. After the Cancel, force a 5 second reset before allowing a new shot.**
- **It takes 5 seconds after shooting for a new frisbee to be in place ready to shoot.**
- **Design shooting logic. Also provide “ready to shoot” digital for dashboard display. Use ONLY the algorithms discussed in this module, and perhaps module 4.**